

Budapest University of Technology and Economics
Department of Electron Devices

Lab. 3

Sequential statements, Processes and Variables

Osama Ali

osamaalisalman.khafajy@edu.bme.hu


Ahmad Halal

ahmadhalalftesah@edu.bme.hu


20 of May 2022

Sequential Statements

 Can be used for building both combinational and sequential logic circuits.




 - The output of the circuit depends solely on the current inputs.
- The system requires no memory and can be implemented using conventional logic gates.



- The output does depend on previous inputs.
- A storage elements are required, which are connected to the combinational logic block through a feedback loop.

 Unlike the concurrent statements, the sequential statements are executed line by line.



This is done by enclosing the sequential statements inside a VHDL construct known as a “**process**”. A “process” can appear anywhere after the “begin” statement of the “architecture”.


Properties of process Statement

- Process statement contains only sequential statements.
- The process statement is itself a concurrent statement.
- A process statement has a declaration section and a statement part.
- In the declaration section, types, variables, constants, subprograms, and so on can be declared.
- The statement part contains only sequential statements.
- All processes in an architecture behave concurrently.

ARCHITECTURE

DECLARATION PART

DEFINITION PART

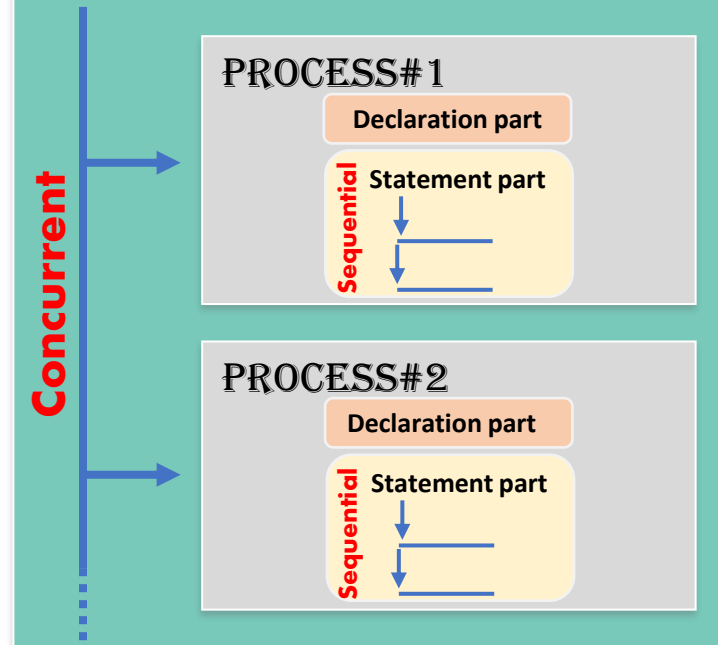

END ARCHITECTURE

Sensitivity List

- The process statement can have an explicit sensitivity list that causes the statements inside the process statement to execute whenever one or more elements of the list change value.
- The process must have an explicit sensitivity list or, a WAIT statement. **OR...?**
- The sensitivity list **should** contain all input signals used in that process.

```
process (A,B)
begin
    if (A='1' or B='1') then
        Z <= '1';
    else
        Z <= '0';
    end if;
end process;
```

```
process
begin
    if (A='1' or B='1') then
        Z <= '1';
    else
        Z <= '0';
    end if;
    wait on A,B;
end process;
```

Signal Assignment Versus Variable Assignment

Signal

```
Architecture beh_1 of test is
    signal A,B,C: integer;
    signal Y, Z : integer;
    signal M, N : integer;
begin
    process (A,B,C,M,N)
    begin
        M <= A;
        N <= B;
        Z <= M + N;
        M <= C;
        Y <= M + N;
    end process;
end Architecture;
```

Variable

```
Architecture beh_1 of test is
    signal A,B,C: integer;
    signal Y, Z : integer;
begin
    process (A,B,C)
        variable M, N: integer;
    begin
        M := A;
        N := B;
        Z <= M + N;
        M := C;
        Y <= M + N;
    end process;
end Architecture;
```

If Statement


- Syntax:

```
if (condition 1) then  
  
elseif (condition 2) then  
  
elseif (condition 3) then  
  
else  
  
end if;
```

- “IF” statement evaluates each condition in order
- Statement can be nested
- **Spaghetti code** (Avoid using more than three levels of **if...else** statements)
- When defining the condition, use parentheses to differentiate levels of operations on the condition

If Statement
 
```
process (sel, a, b, c, d)
begin
  if sel(2) = '1' then
    y <= a;
  elsif sel(1) = '1' then
    y <= b;
  elsif sel(0) = '1' then
    y <= c;
  else
    y <= d;
  end if;
end process
```



Generates a priority structure.


Corresponds to “when-else” command in the concurrent part.

Case Statement

- Syntax:

```
case expression is
    when choice1 => {statements}
    when choice2 => {statements}
    when others => {statements}
End case;
```
 
```
process (sel, a, b, c, d)
begin
  case sel is
    when "00" => Y <= a;
    when "01" => Y <= b;
    when "10" => Y <= c;
    when others => Y <= d;
  end case;
end process;
```



- “Case” statement is a series of parallel checks to check a condition.
- Statements following each “when” clause is evaluated only if the choice value matches the expression value.
- Corresponds to “with...select” in concurrent statements

Process statement

- Two types of processes
 - Combinatorial (asynchronous)
 - Clocked (synchronous)

Combinatorial Process (asynchronous)

- Generates combinational logic.
- All inputs must be present in the sensitivity list.

```
process (a, b, c)
begin
    x <= (a and b) or c;
end process;
```

Clocked Process (synchronous)

Any signal assigned under a clk' event generates a flip-flop


```
process (clk)
begin
    if (clk' event and clk = '1') then
        Q <= Data;
    end if;
end process;
```



- Clocked processes having an “else” clause will generate wrong hardware.

Bad Hardware Description

 
```
process (clk)
begin
    if (clk' event and clk = '1') then
        out1 <= a and b;
    else
        out1 <= c;
    end if;
end process;
```



Synchronous

- Synchronous Reset: Flip-flops are reset on the active edge of the clock when reset is held active.

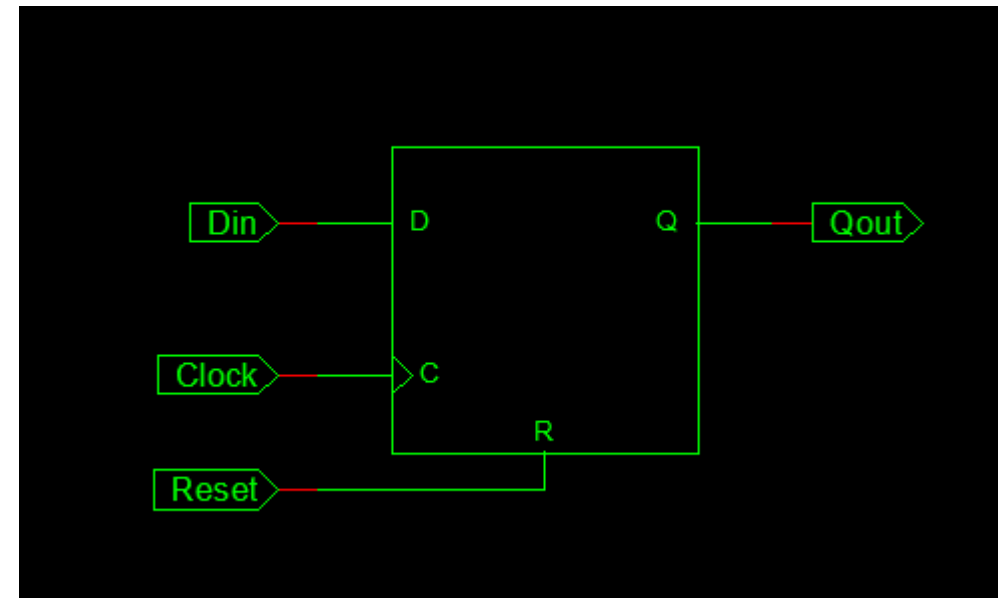
```
process (clk)
begin
    if (clk' event and clk = '1') then
        if (Reset = '1') then
            Q <= '0';
        else
            Q <= D;
        end if;
    end if;
end process;
```



Asynchronous

- Asynchronous Reset: Flip-flops are cleared as soon as reset is asserted.
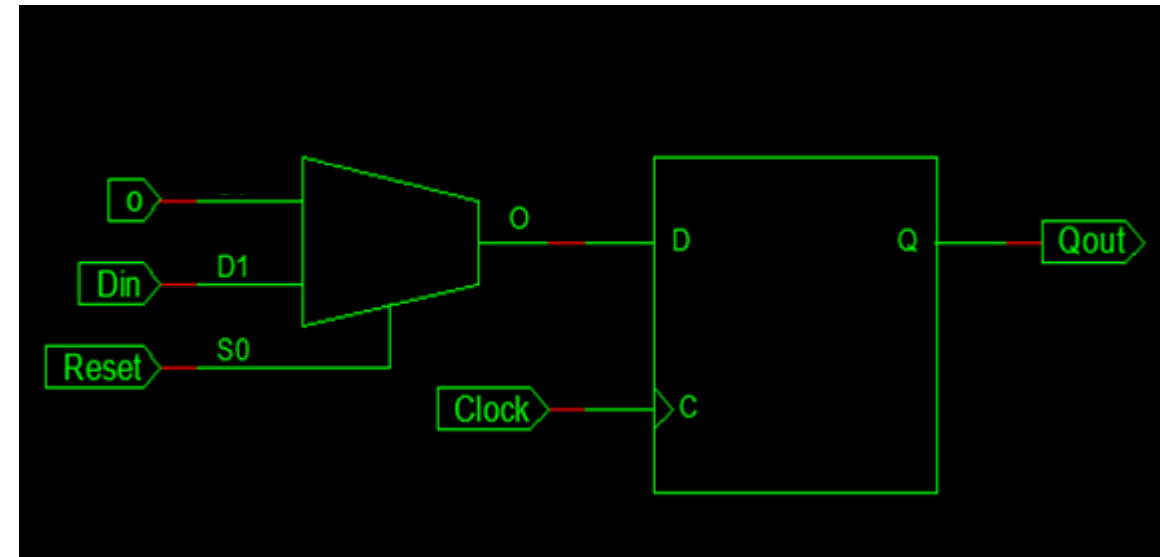
```
PROCESS (clk, rst)
BEGIN
    IF (clk'EVENT AND clk='1') THEN
        IF (rst='1') THEN
            q1 <= '0';
        else q1 <= d;
        END IF;
    END IF;
END PROCESS;
```



Clock generation in the testbench

```
library ieee;
use ieee.std_logic_1164.all;

entity Lab_4 is
end Lab_4;

architecture TEST_behavior of Lab_4 is

-- Insert component declaration for device under test (DUT) here.

-- Insert signal declarations here.

SIGNAL CLKK : STD_LOGIC := '0';
SIGNAL RST : STD_LOGIC := '0';
SIGNAL D : STD_LOGIC := '0';

begin
-- Clock Generation
CLKK <= NOT CLKK AFTER 10 NS;
-- Insert component instantiation (i.e. port map statement) here.

    stimulus: process
    begin


        -- Insert your testbench code here.

    end process;

end TEST_behavior;
```

Write a VHDL code that can model the below Circuit of D flip-flop using behavioral modeling.

 - The circuit consists of two D_flip-flops one with **synchronous reset** and **one without**.
- Create a new project and label it as “Lab_5_1”
- Download the VHDL testbench file (TestBench_Lab5.vhd.). Develop it to test and analyze the design behavior.



Write a VHDL code that can model the below Circuit of D flip-flop using behavioral modeling.

- The circuit consists of two D_Flip-flops one with **Asynchronous reset** and **one without**.
- Create a new project and label it as “Lab_5_2”
- Download the VHDL testbench file (TestBench_Lab5.vhd.). Develop it to test and analyze the design behavior.

