 



Microelectronics, BSc course

**nMOS/CMOS Logic Gates II:
Schematic, layout, x-section, std
cells**

The abstraction level of our study:




The CMOS inverter – recall

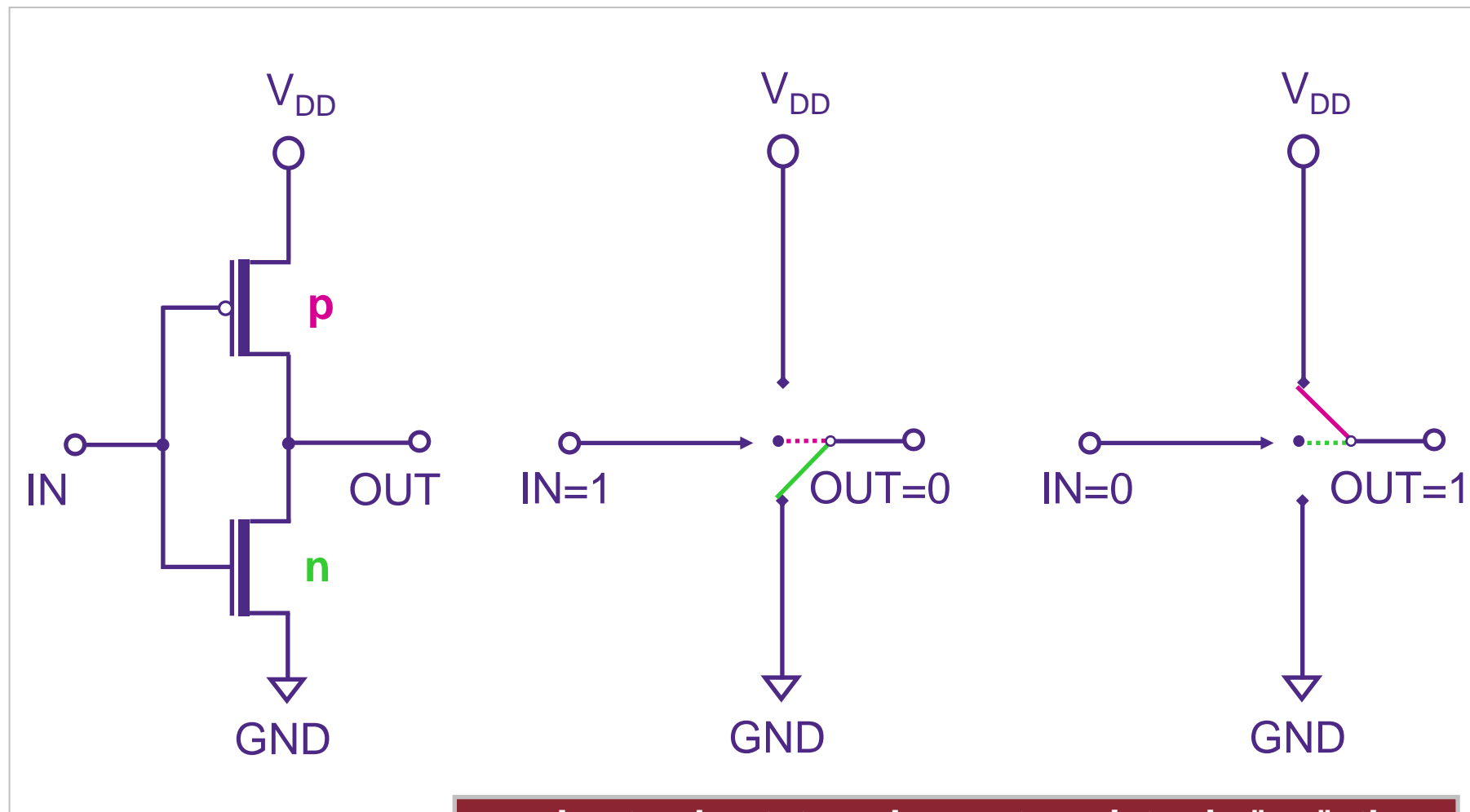




In steady-state only one transistor is "on", the other one is always "off"

X-sectional view of a CMOS inverter

 

Characteristic of the CMOS inverter

   2 basic cases, depending on the **supply voltage** and threshold voltages of the transistors



1. small supply voltage:

$$V_{DD} < V_{Tn} + |V_{Tp}|$$

only one transistor is "on" at a time

2. larger supply voltage:


$$V_{DD} > V_{Tn} + |V_{Tp}|$$

when switching over, both transistors are "on" at the same time

Characteristic of the CMOS inverter

- 1. **small supply voltage:** $V_{DD} < V_{Tn} + |V_{Tp}|$

the characteristics: $U_{OUT} = \begin{cases} V_{DD} & \text{if } U_{IN} < V_{DD} - |V_{Tp}| \\ \text{indefinit} & \text{if } V_{Tn} < U_{IN} < V_{DD} - |V_{Tp}| \\ 0 & \text{if } U_{IN} > V_{Tn} \end{cases}$

 


The middle part of the transfer characteristic is very steep, this is the specific advantage of CMOS inverters.

Characteristic of the CMOS inverter

- 2. **large supply voltage:** $V_{DD} > V_{Tn} + |V_{Tp}|$
Switching over? - "mutual conduction"

► Constructing the characteristic:

 

The CMOS inverter

Design for symmetrical operation:

If $U_{IN}=U_{inv}$ logic threshold voltage, both transistors have equal current:

$$K_n(U_{inv} - V_{Tn})^2 = K_p(U_{DD} - U_{inv} - |V_{Tp}|)^2$$

$$U_{inv} = \frac{U_{DD} - |V_{Tp}| + V_{Tn} \sqrt{K_n / K_p}}{1 + \sqrt{K_n / K_p}}$$

$$K_x = \left(\frac{W}{L} \right)_x \frac{\mu_x C_{ox}}{2}$$

$$U_{GSn} = U_K$$

$$U_{GSp} = V_{DD} - U_K$$

The inverter logic threshold voltage depends on the ratio of the current constants of the transistors.



To have U_{inv} at $V_{DD}/2$ and $V_{Tn}=|V_{Tp}|$, then $K_n=K_p$ has to be set.

$$\left(\frac{W}{L} \right)_P = 2..2.5 \times \left(\frac{W}{L} \right)_n \quad \text{since hole mobility is 2 ... 2.5 times less}$$

The logic threshold voltage can be set by the W/L ratios

The CMOS inverter / dynamic char.

  
- Calculation of the switching times
 - What do they depend on?
 - the current driving capability of the output
 - the capacitive load on the output



- If the characteristics of the two transistors are exactly complementary ($K_n = K_p$ and $V_{Tn} = |V_{Tp}|$), rising and falling times will be equal

The capacitances

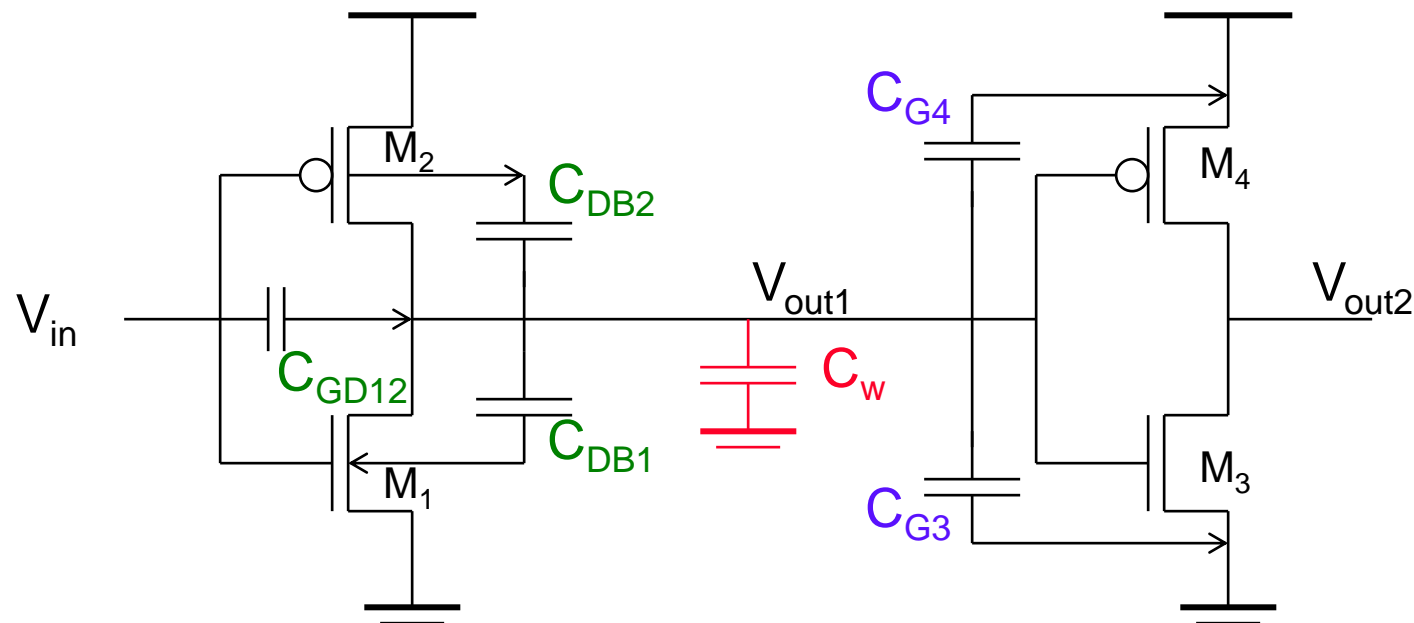- Intrinsic capacitances of the driving stage
- Input capacitance of the loading stage (next gate) – extrinsic or fanout capacitances
- wiring (interconnect) capacitance



intrinsic MOS transistor capacitances


extrinsic MOS transistor (fanout) capacitances

wiring (interconnect) capacitance

The capacitances

■ The intrinsic capacitances:


 
- S-G G-D overlap capacitances
- the MOS capacitance of the channel
- capacitances of pn junctions



■ The wiring capacitance

- depends on the interconnect geometry (width, length)
- with the advance of manufacturing processes this capacitance tends to increase

Modern metallization

  

Intel 0.25 μm process


5 metal layers

Ti/Al - Cu/Ti/TiN

Polysilicon dielectric


<u>LAYER</u>	<u>PITCH</u>	<u>THICK</u>	<u>A.R.</u>
Isolation	0.67	0.40	-
Polysilicon	0.64	0.25	-
Metal 1	0.64	0.48	1.5
Metal 2	0.93	0.90	1.9
Metal 3	0.93	0.90	1.9
Metal 4	1.60	1.33	1.7
Metal 5	2.56	1.90	1.5
	μm	μm	

Layer pitch, thickness and aspect ratio

 

Interconnect capacitances

 Interconnect - substrate: *parallel plate capacitance*




Dielectric
constant
(SiO₂ => 3.9)

$$C_{pp} = (\epsilon_{di}/t_{di}) WL$$


Interconnect capacitances
 
$$\begin{aligned}
 C_{\text{wire}} &= C_{\text{pp}} + C_{\text{fringe}} + C_{\text{interwire}} \\
 &= (\epsilon_{\text{di}}/t_{\text{di}})WL \\
 &\quad + (2\pi\epsilon_{\text{di}})/\log(t_{\text{di}}/H) \\
 &\quad + (\epsilon_{\text{di}}/t_{\text{di}})HL
 \end{aligned}$$



Other issues of interconnects

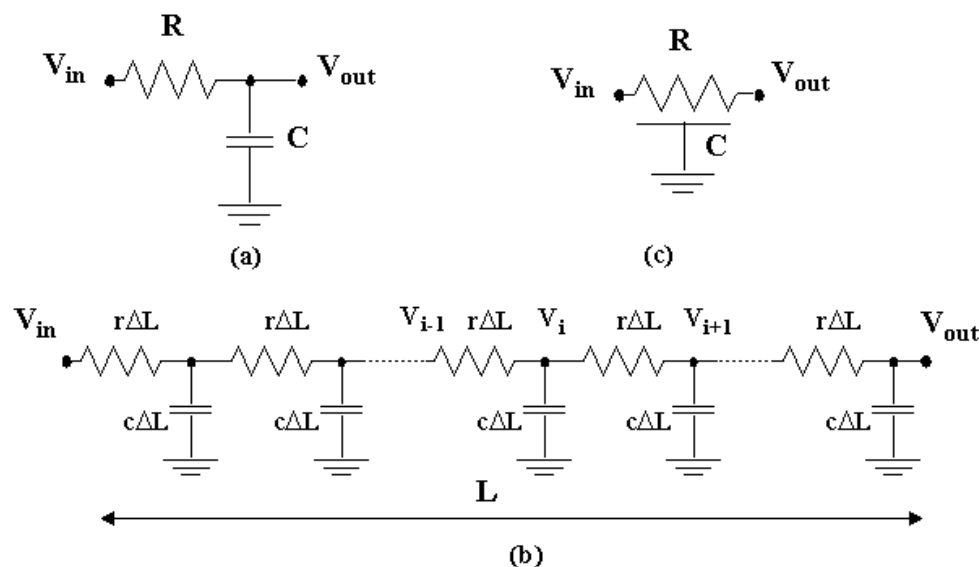- Series resistance
- Distributed parameter RC line (see transmission lines)



Sort of a representation of the diffusion equation


$$rc \frac{\partial V}{\partial t} = \frac{\partial^2 V}{\partial x^2}$$

$$\tau(V_{out}) = \frac{rc L^2}{2}$$

The CMOS inverter / dynamic char.

■ Calculation of switching times

 - identical times, integration for the extreme values of the voltage of the load capacitance:



$$t_l = \int_{V_{DD}}^{V_{LM}} \frac{C_L}{I_D} dU$$

■ If

$$I_D \approx K(V_{DD} - V_T)^2$$

V_{LM} – minimal voltage of the load capacitance

then

$$t_l = \frac{C_L (V_{DD} - V_{LM})}{K (V_{DD} - V_T)^2}$$

Can be reduced by increasing the supply voltage or the W/L ratio

Power consumption of CMOS inv.

- **There is no static consumption** since there is no static current
- There is **dynamic consumption** during switching which consists of 2 parts:
 - **Mutual conduction:**
 - During the rise of the input voltage both transistors are "on"

$$V_{Tn} < U_{IN} < V_{DD} - V_{Tp}$$


- **Charge pumping:**
 - At switching over the output to 1 the $C_{L \text{ loading}}$ capacitor is charged to the supply voltage through the p transistor, then it is discharged towards the ground through the n transistor.

Charge is pumped from VDD to GND.

Power consumption of CMOS inv.:

■ Mutual conduction ("short power"):

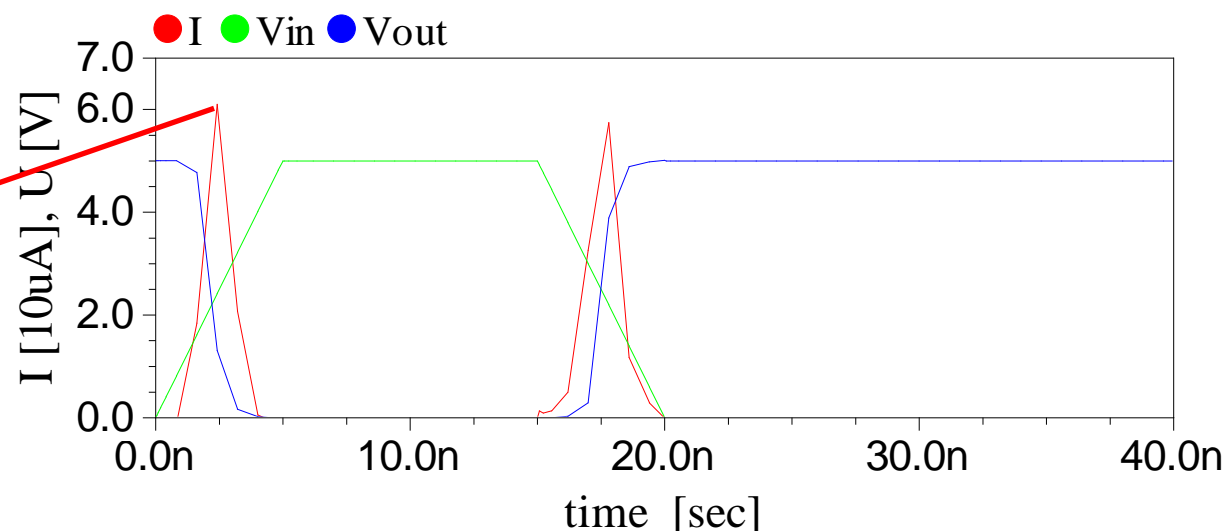- During a certain period of the rise of the input signal both transistors are "on" if $V_{Tn} < U_{IN} < V_{DD} - V_{Tp}$ this is called mutual conduction



$$I_{MAX} = K(V_{DD} / 2 - V_T)^2$$

- charge flowing through: $\Delta Q = b t_{UD} I_{MAX}$, where t_{UD} is the time while current is flowing, b is a constant depending on the signal shape. $b \approx 0.1-0.2$

$$P = f \Delta Q V_{DD} = f V_{DD} b t_{UD} K (V_{DD} / 2 - V_T)^2$$

$$P \sim f V_{DD}^3$$

Power consumption of CMOS inv.:

▪ Charge pumping:

- At switching the C_L load capacitance is charged to VDD through the p-channel device when the output changes to 1, later, when switching the output to 0, it is discharged towards GND through the n-channel device.


$$\Delta Q_L = C_L V_{DD}$$

$$P_{cp} = f C_L V_{DD}^2$$

- The power consumption due to charge pumping is proportional to **the frequency and the square of the supply voltage**.
- **Total consumption:** sum of the two components (if there is mutual conduction), directly proportional to the **frequency** and the 2nd and 3rd power of the supply voltage.

Components of the consumption of CMOS circuits

 - Dynamic components – at every switching event
 - mutual conduction, charge pumping
 - proportional to the event density
 - clock frequency
 - circuit activity




- Further components due to parasitics:
 - subthreshold currents
 - leakage currents of pn junctions – nowadays already significant
 - leakage (tunneling) through the a gate dielectric

Construction

- ▶ Constructing CMOS gates on schematic (circuit) level
- ▶ Process and layout
 - ▶ Recall the nMOS process and layout
 - ▶ Stick diagram layout
 - ▶ Full layout
 - ▶ Create standard cells

CMOS gates

- **PDN**: Create an nMOS switching circuit (pull down network):
 - series path: NAND function
 - parallel path: NOR function
 - combination of these: complex gate
 - Switches: **nMOS** transistors
- **PUN**: *Load of the former nMOS gates with no active control is replaced by a full network: the dual circuit of the nMOS pull down network:*
 - Dual topology (series \rightarrow parallel, parallel \rightarrow series, aka the loop-cut duality)
 - Dual component: **pMOS** transistors
- The transistor gates in the PDN and PUN receive the **same control signals** (inputs)

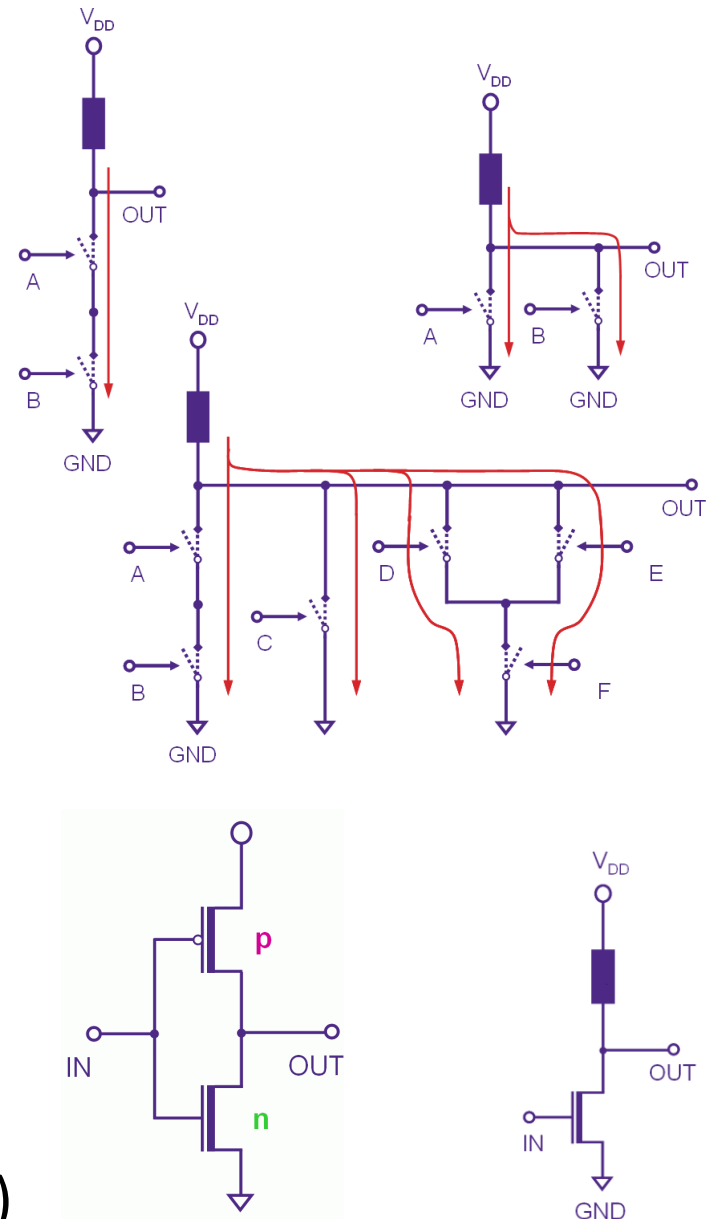

CMOS gates


- In a CMOS inverter both transistors are actively controlled
- In case of gates there will be a PUN (pull up network: pMOS circuit) and a PDN (pull down network: nMOS circuit). The number of transistors both in PUN and PDN is equal to the number of inputs of the gate
 - For input combinations where the output is 0, the PDN realizes a short towards GND and the PUN is an open circuit;
 - if the output function is equal to 1, the PDN will be an open circuit and the PUN realizes a short towards VDD.

Circuits with dual topology should be realized from n and p channel transistors

- Gates of transistors receiving the same signal are connected

CMOS gates


- NOR gate
- NAND gate

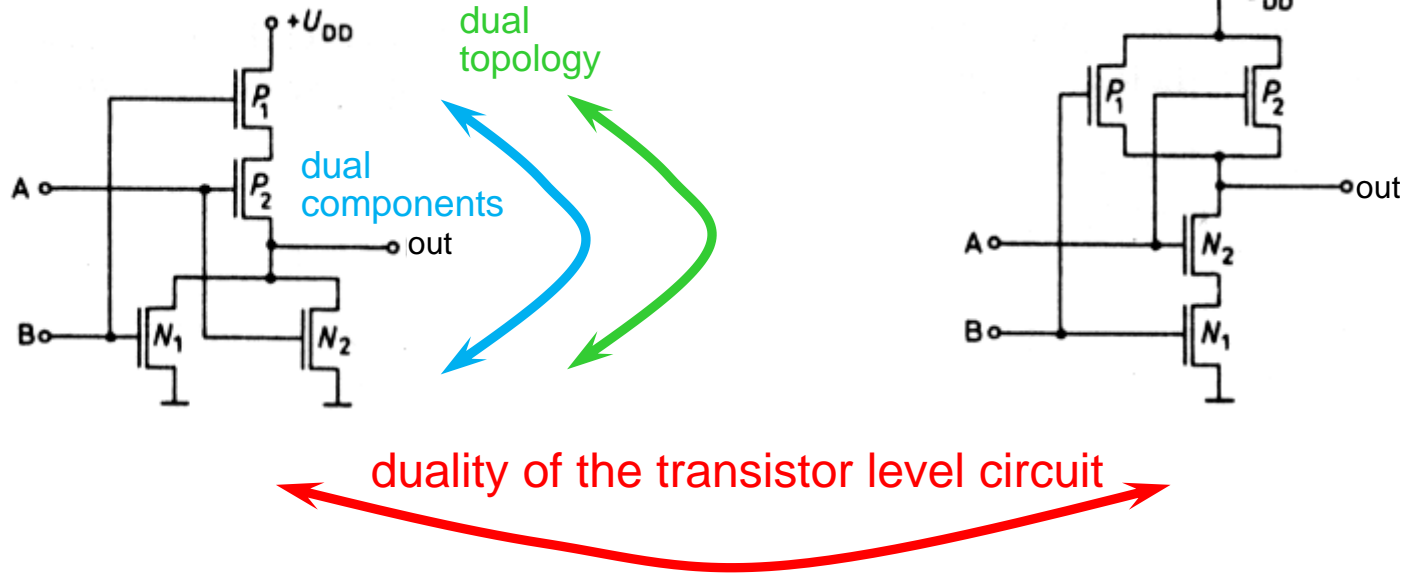

For an n input CMOS gate $2n$ transistors are needed
(passive load gates need only $n+1$ transistors)


Construction complex CMOS gates

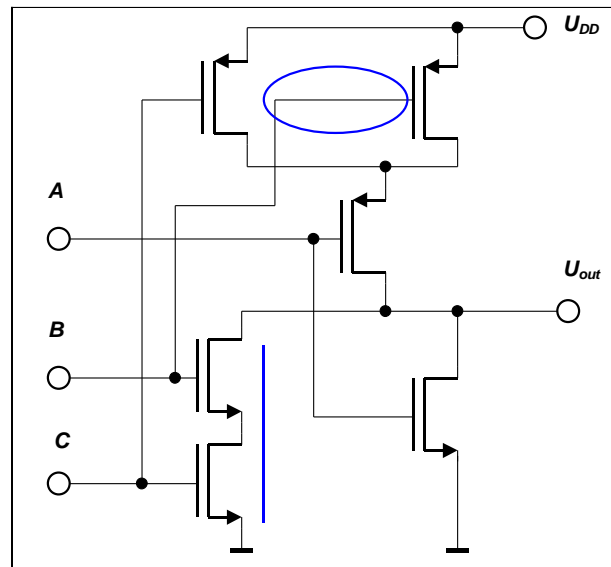- dual topology (loop \Rightarrow cut, cut \Rightarrow loop)
- dual components: nMOS replaced by pMOS
- transistor gates corresponding to the same signal must be connected
- proper sizing of the W/L ratios (electron/hole mobility mismatch)



$$F = \overline{A + BC}$$

The abstraction level of our study:

 


Metal gate MOS transistor

Layout view:

 Problems:

- metal gate – large V_T
- requires accurate mask alignment




Poly-Si gate MOS transistor

In-depth structure:

Layout view:


Advantages

- smaller V_T
- self alignment

 

A poli-Si gate nMOS process

 
- ▶ Start with: p type substrate (Si wafer)
 - cleaing,
 - grow thick SiO_2 – this is called *field oxide*




A poli-Si gate nMOS process

► Create the active zone with photolithography

 - coat with resist,
- expose to UV light through a mask,
- development, removal of exposed resists
- etching of SiO_2 removal of the resist




M1: active zone

 


A poli-Si gate nMOS process

► Create the gate structure:

 - growth of thin oxide
- deposit poly-Si
- pattern poly-Si with photolithography (resist, exposure, develop)
- etch poly-Si, etch thin oxide



M2: poly-Si pattern

 


A poli-Si gate nMOS process

► S/D doping (implantation)

- the oxide (thin, thick) masks the dopants
- this way the self-alignment of the gate is assured


► Passivation: deposit PSG

 

A poli-Si gate nMOS process

► Open contact windows through PSG

 - photolithography (resist, expose pattern, develop)
- etching (copy the pattern)
- cleaning




M3: contact window pattern

A poli-Si gate nMOS process

► Metallization

 - Deposit Al
- photolithography, etching, cleaning




M4: metallization pattern

- The recipe of the process is given, the in-depth structure is determined by the sequence of the masks
- One needs to specify the shapes on the masks
 - ***The set of shapes on subsequent masks is called layout***

A poli-Si gate nMOS process

Structure (x-sectional view):

 


Source/drain doping

thin oxide

poli-Si gate

metallization,
contact window


Layout (top
view):

 

Steps of the self-aligned poli-Si gate process

- 1) Open window for the active region M
 - photolithography, field oxide etching
- 2) Growth of thin oxide
- 3) Window for hidden contacts M
 - Contacts the poli-Si gate (yet to be deposited) with the active region (after doping).
- 3) Deposit poli-Si
- 4) Patterning of poli-Si M
- 5) Open window through the thin oxide (etching only)

Layout of a depletion mode inverter



 


- Layout == set of 2D shapes on subsequent masks
- Masks are color coded:
 - active zone: red
 - poly-Si: green
 - contact windows: black
 - metal: blue
- Mask == layout layer

Where is a transistor? Channel between two doped regions:

CHANNEL = ACTIVE AND POLY

Simplified layout: *stick diagram*

   

Si-compilers

- Logic schematic / netlist / high level description
- Transistor level schematic with W/L information
- Stick diagram layout
- Actual layout
 - Automatic conversion between these representations
 - HARDWARE SYNTHESIS
 1. From behavioural description structural description
 2. Implementation of the structural description with a given realization mode / manufacturing process: *technology mapping*
 - *We have seen basics of the realization of an application specific integrated circuit (ASIC)*
 - *Designs can also be mapped to an FPGA*


Layout primitives: simple shapes



Active zone (window opening through the oxide)



Gate (mask of poly-Si pattern)

 


Contacts (window opening mask through oxide/PSG)




S/D lines (mask of metallization pattern)


Layout macros – from primitives

 

 layout of an nMOS transistor: *layout primitives on actual layers corresponding to real masks*




nMOS transistor layout + outline + pins

 

nMOS transistor macro:


outline, pins, scripts: *pseudo layers*

 Layout macros – from macros and primitives



Gate level layout


CMOS structure (inverter)

 

CMOS structures


- Further masks:
 - n-well (or p-well, depending on the substrate)
 - p doping (or n doping, depending on the substrate)
- Multiple metal layer CMOS:
 - each metallization needs own mask,
 - contact windows, vias
- There could be multiple poly-Si layers (analog CMOS)
- Typically: 15..20 masks
- Certain rules need to be kept for manufacturability: **design rules**
 - ***come from the process, given by Si-foundry***

Layout of a CMOS inverter

 

Standard cells of gates

 - The CMOS inverter layout shown before has also been created according to conventions of standard cell design





Standard cells


- In layout view one can refer to the inverter through its layout macro (cell outline and pins)




Standard cells

  


Standard cella in a row:

 


Standard cell IC:

 

Detail of a standard cell IC:

 

Details of a CMOS circuit

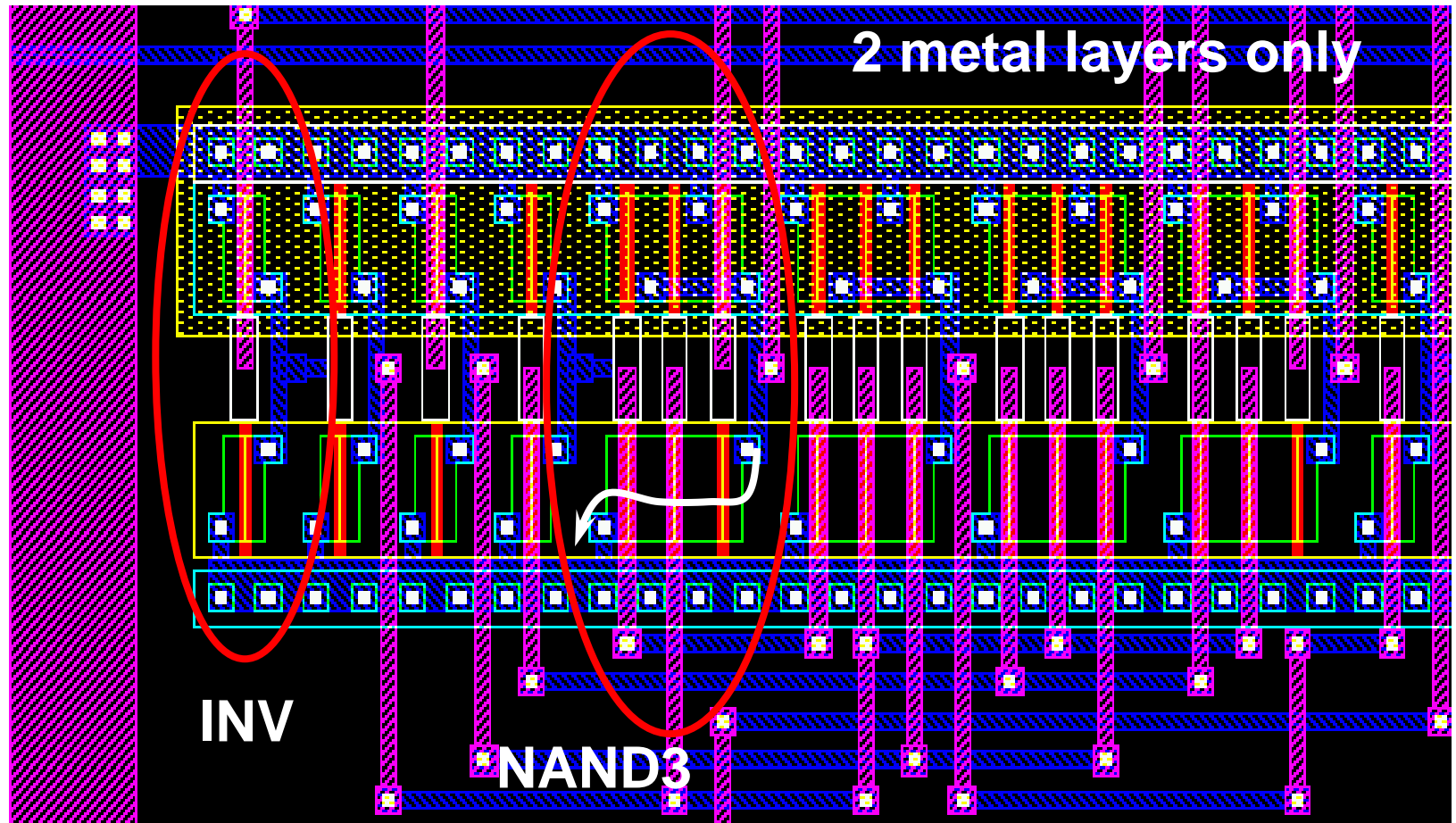

Layout extraction: checking, real delays

The same in CAD tools of VLSI design

