

Microelectronics, BSc course




nMOS/CMOS Logic Gates

Overview of MOSFET types

Type	Circuit Symbol	Cross Section	Output Characteristics	Transfer Characteristics
n-Channel Enhancement (Normally Off)				
n-Channel Depletion (Normally On)				
p-Channel Enhancement (Normally Off)				
p-Channel Depletion (Normally On)				


Char. of enhancement mode n type MOSFETs

Now we calculate with this!

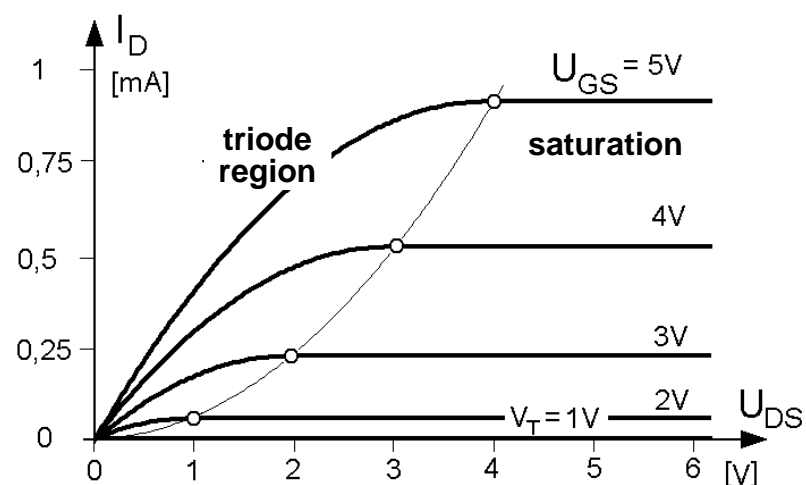  


Simple model of MOSFETs

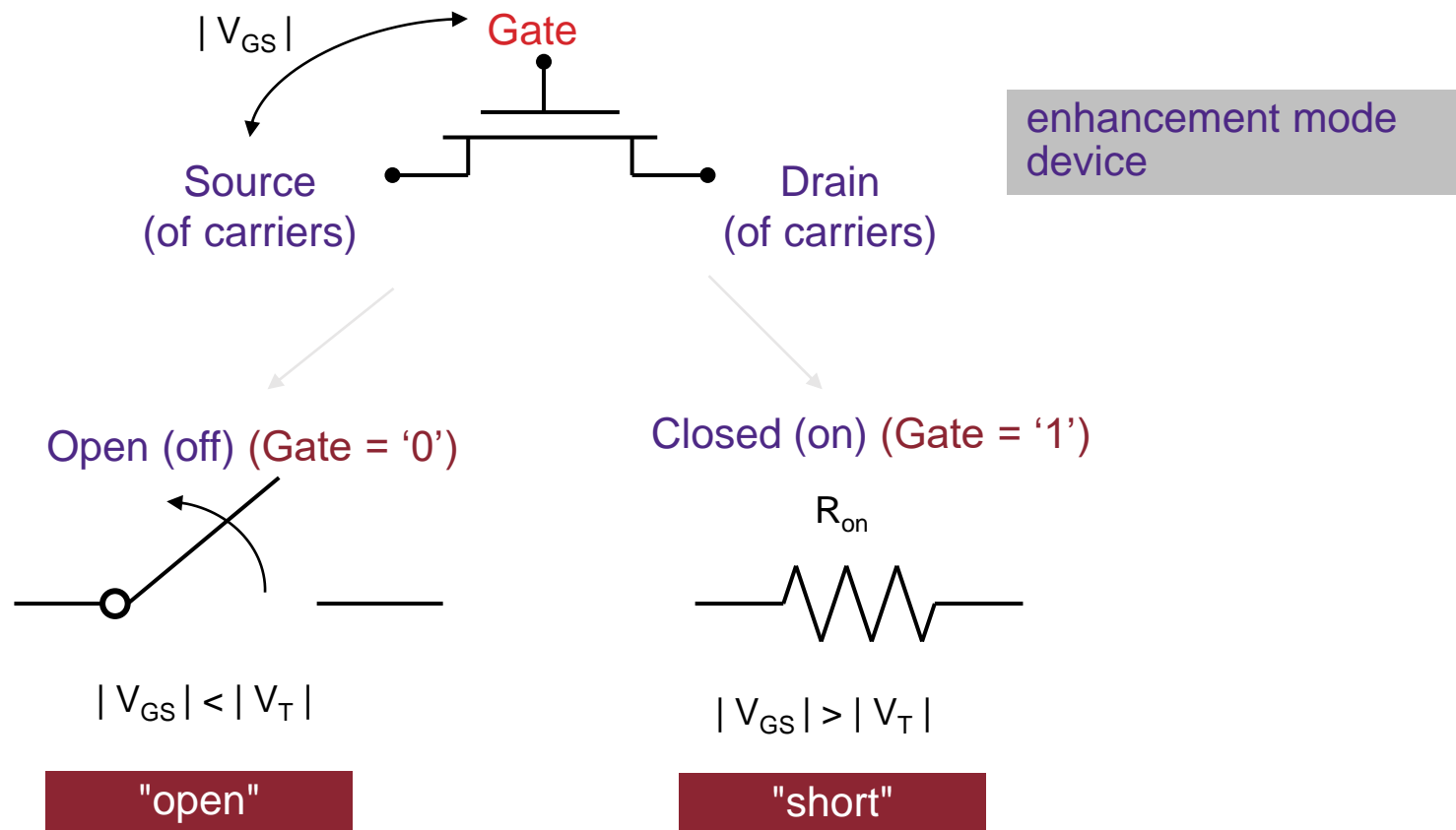- The simplest (**logic**) model:
 - **no conduction** (off) / **conduction** (on)



Let's construct an inverter!

 
- Resistor at supply voltage (V_{DD})
- Other end connected to ground (GND) through a switch
- Switch controlled by a logic signal:
 - 1 (V_{DD} level) – "short"
 - 0 (GND level) – "open"
- The output is the common node of the switch and the resistor



Let's construct an inverter!


► IN = 1

 - switch "on"
- output connected to GND
- **OUT = 0**




► IN = 0

 - switch "off"
- output floating at V_{DD}
- **OUT = 1**



Two switches in series: NAND gate

 


► If A and B equal to 1, then $OUT=0$

► This is the NOT (A AND B) function, i.e. NAND

In practice with max. 3..4 inputs.

If there are *parallel* conduction paths then we get the *NOR function*

The scheme of the NOR gate:

 

PARALLEL
conduction path


► If A or B equals to 1, then $OUT=0$

► This is the NOT (A OR B) function, i.e. NOR

Complex conduction paths == option for complex logic gates

Complex logic gates




- Serial paths connected in parallel

 

Inverter realizations

Switch = n channel MOSFET: *normally OFF device*

   Load resistor: another transistor, e.g. in triode region




Needs another supply – **not OK**

nMOS technique – very simple


- Simple process, outdated, many disadvantages
 - static consumption if $OUT=0$
 - if $OUT = 0$, it will not be a pure GND level
 - asymmetrical transfer characteristic (see later)

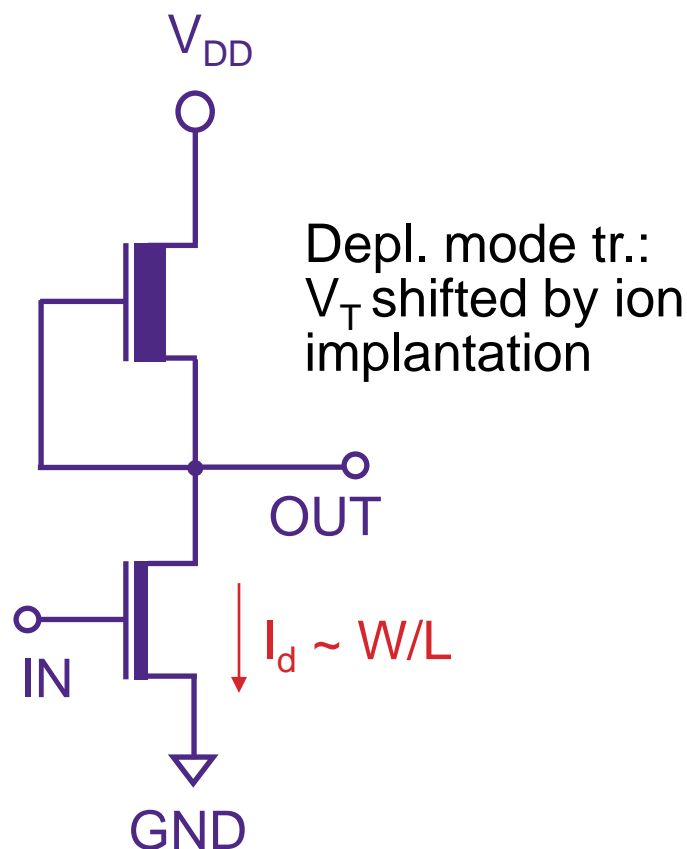- In both cases the *load* resistor is replaced by a MOSFET but this transistor was not provided with an active control
 - *This is the passive load inverter*



Complex gates (in nMOS)

 - Serial conduction paths in parallel, e.g.:



There are 4 paths


$$OUT = \overline{AB + C + (D + E)F}$$

The CMOS technique



- The name comes from: **C**omplementary **MOS**
- Idea: the load also should be provided with active control
 - **if** the nMOS *driver* (switching) transistor conducts, **then** the *load* transistor must be an "open" circuit
 - **if** the nMOS *driver* (switching) transistor is an "open circuit", **then** the *load* must be conducting
- This needs such a *normally OFF device* which needs "opposite" control signals than the nMOS transistors
 - Such device is an enhancement mode **pMOS transistor**

The CMOS inverter

 - An n and a p type enhancement mode device
- **Active load inverter**: the two transistors have the **same common control**



  In steady state only one device is "on", the other is "off".




Characteristics of inverters, rudiments

- Transfer characteristic:
 - output voltage vs. input voltage



$$U_{out} = f(U_{in})$$

 The output signal is the inverted version of the logic value of the input signal



transfer characteristic of an ideal and a realistic inverter

Xfer char. of a CMOS inverter

  


$$U_{IN} = U_{GSn} \quad U_{OUT} = U_{DSn}$$

Characteristics of inverters, rudiments

■ Noise immunity:

 - Same U_{out} corresponds to a wide U_{in} range
- There are 3 regions in the characteristic
- On the L and H sides the characteristic is flat, i.e. any voltage change in the input has negligible effect on the output.





L and H regions

transfer characteristic of an ideal and a realistic inverter

Characteristics of inverters, rudiments

- Signal regeneration
 - depends on the slope of the middle region

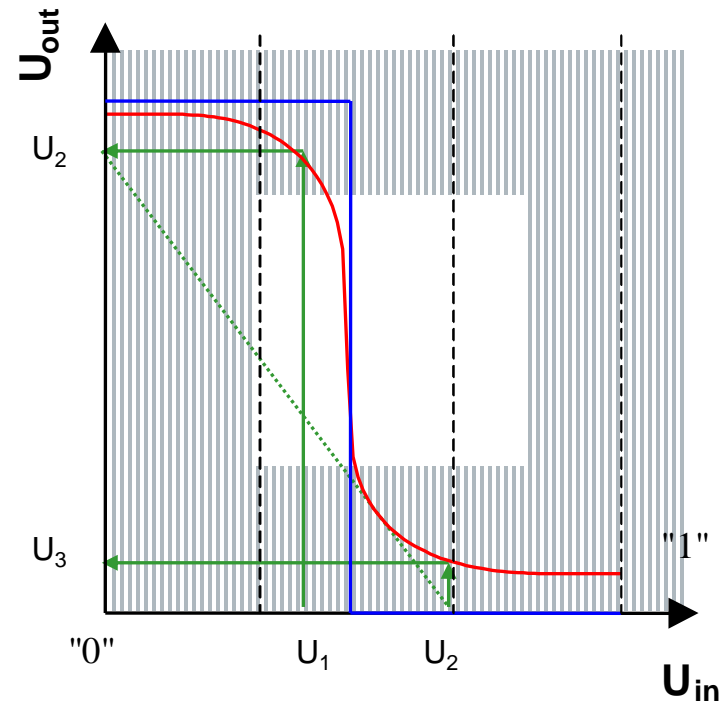 
U_1 is a "bad" logic 0 signal. Output U_2 of the first inverter is already close to an acceptable logic 1 level. output voltage U_3 at the second inverter is already a "good" logic 0 level.




transfer characteristic of an
ideal and a realistic inverter

Characteristics of inverters, rudiments

- Signal regeneration

 

$$U_L = 0V, U_H = 5V$$

 

(SPICE simulation)


In case of U_3 both the voltage level and the signal form are visibly regenerated!

Characteristics of inverters, rudiments

- Inverter logic threshold voltage

The level, under which the signals will be converted into logical 0 and above which the signals will be converted by the inverter chain into logical 1

 Intersection of the $U_{in}=U_{out}$ line and the x-fer characteristic



Characteristics of inverters, rudiments

■ Logic level ranges


The voltage range of the logic 0 and 1 values **within** which the circuit works safely in the respective logic level

Example: 74HC00,

$V_{dd}=3V$,

$U_{LM}=0.9V$

$U_{Hm}=2.1V$

 


Important voltage values

U_{LM} , max. of logic 0

U_{Hm} , min. op logic 1

Characteristics of inverters, rudiments


- Propagation delay

 

t_{pd} is difficult to define, and may be different for switching on and off (e.g. nMOS inverters)


Characteristics of inverters, rudiments

■ Inverter pair delay

 

A long chain of uniform inverters is assumed. After a certain number of inverters the signal form will be determined by the inverter properties only.

 After propagating through 2 inverters the signal will be the same, the delay will be t_{pdp} – the inverter **pair propagation delay**




Characteristics of inverters, rudiments

- Measuring the inverter pair delay

THE RING OSCILLATOR

 Odd number of inverters connected in a chain, no stable state \Rightarrow oscillation



$$T = n \cdot t_{pd}$$

Characteristics of inverters, rudiments

- Power-delay product ($P\tau$)
 - **low power** and **small delay** refer to good quality,
 - their product is a **figure of merit** for the quality of a circuit family.
 - the physical meaning: the minimal energy, needed to work on 1 bit of information.

